

# 2016 EE214B Design Project - Part I

Singireddy, Sanjana  
sanjana9@stanford.edu  
SUID:06030068

Lenius, Samuel  
lenius@stanford.com  
SUID:06091240

February 29, 2016

# 1 Bias Calculations

## 1.1 Node Definitions

$$V_{C1} = V_{E2} = V_W$$

$$V_{B3} = V_{C2} = V_{B4} = V_X$$

$$V_{E3} = V_Y$$

$$V_{E4} = V_Z$$

$$V_{B1} = V_{IN}$$

## 1.2 Node Voltages and Device Currents

$$V_{IN} = V_{BE} = 0.8V \quad (1)$$

$$V_{B2} = 1.6V \Rightarrow V_W = 1.6 - V_{BE} = 0.8V \quad (2)$$

Assuming  $I_b = 0$

$$V_{IN} = V_Y \Rightarrow V_Y = 0.8V \quad (3)$$

$$V_X = V_Y + V_{BE} \Rightarrow V_X = 1.6V \quad (4)$$

$$V_Z = V_X - V_{BE} \Rightarrow V_Z = 0.8V \quad (5)$$

$$V_O = V_{CC} - I_{B4}R_{C4} \Rightarrow V_O = 2.3V \quad (6)$$

$$I_{C1} = I_{C2} = \frac{V_{CC} - V_{B3}}{R_{C2}} = 3.6mA \quad (7)$$

$$I_{C3} = I_{Bias3} = 4.5mA \quad (8)$$

$$I_{C4} = I_{Bias4} = 2.0mA \quad (9)$$

Parameter	Hand Calc	Spice Value	Percent Error%
$V_{IN}$	0.800V	0.801V	-0.12%
$V_W$	0.800V	0.798V	0.25%
$V_X$	1.600V	1.605V	-0.31%
$V_Y$	0.800V	0.804V	-0.49%
$V_Z$	0.800V	0.813V	-1.50%
$V_O$	2.300V	2.301V	-0.04%
$gm_1$	120.7mS	120.7mS	-0.03%
$gm_2$	120.3mS	120.3mS	-0.03%
$gm_3$	152.3mS	152.3mS	0.02%
$gm_4$	70mS	70mS	-0.04%
$r\pi_1$	2.14k $\Omega$	1.875k $\Omega$	14.3%
$r\pi_2$	2.14k $\Omega$	1.883k $\Omega$	13.64%
$r\pi_3$	1.71k $\Omega$	1.502k $\Omega$	13.84%
$r\pi_4$	3.85k $\Omega$	3.515k $\Omega$	9.5%

## 2 Calculations and plots for part I (c) through (f)

(c) Applying two-port analysis for loop gain calculation gives:

$$a = (r_{\pi 1} || R_F) \cdot (-gm_1 R_{C2}) \cdot \frac{gm_3 R_F}{1 + gm_3 R_F} = -5.486k\Omega \quad (10)$$

$$f = \frac{-1}{R_F} = -4.5mS \quad (11)$$

$$T_0 = af = 26.57 = 28.48dB \quad (12)$$

Mid-band transresistance of the overall amplifier:

$$A_{CL, MidBand} = \frac{a}{1 + T_0} \cdot \frac{-gm_4 R_{C4}}{1 + gm_4 R_{E4}} = 724 = 57.2dB \quad (13)$$

(d) Calculating node resistances and capacitances to estimate the poles at the nodes:

At node X,  $C_{\pi 3}$ ,  $C_{\pi 4}$ ,  $r_{\pi 3}$  and  $r_{\pi 4}$  will be bootstrapped due to the presence of emitter degeneration resistances.

Miller approximation was applied to  $C_{\mu 4}$

$$C_X = C_{\mu 2} + \frac{C_{\pi 3}}{1 + gm_3 R_F} + \frac{C_{\pi 4}}{1 + gm_4 R_{E4}} + C_{\mu 3} + C_{\mu 4}(1 + gm_4 R_{C4}) = 99fF \quad (14)$$

$$R_X = R_{C2} || r_{\pi 3}(1 + gm_3 R_F) || r_{\pi 4}(1 + gm_4 R_{E4}) = 241\Omega \approx R_{C2} \quad (15)$$

$$C_{IN} = C_D + C_{\pi 1} + C_{\mu 1} = 324fF \quad (16)$$

$$R_{IN} = r_{\pi 1} || R_F = 199\Omega \approx R_F \quad (17)$$

The two most significant poles are given by:


$$f_{IN} = \frac{1}{2\pi R_{IN} C_{IN}} = 2.46GHz \quad (18)$$

$$f_X = \frac{1}{2\pi R_X C_X} = 6.63GHz \quad (19)$$

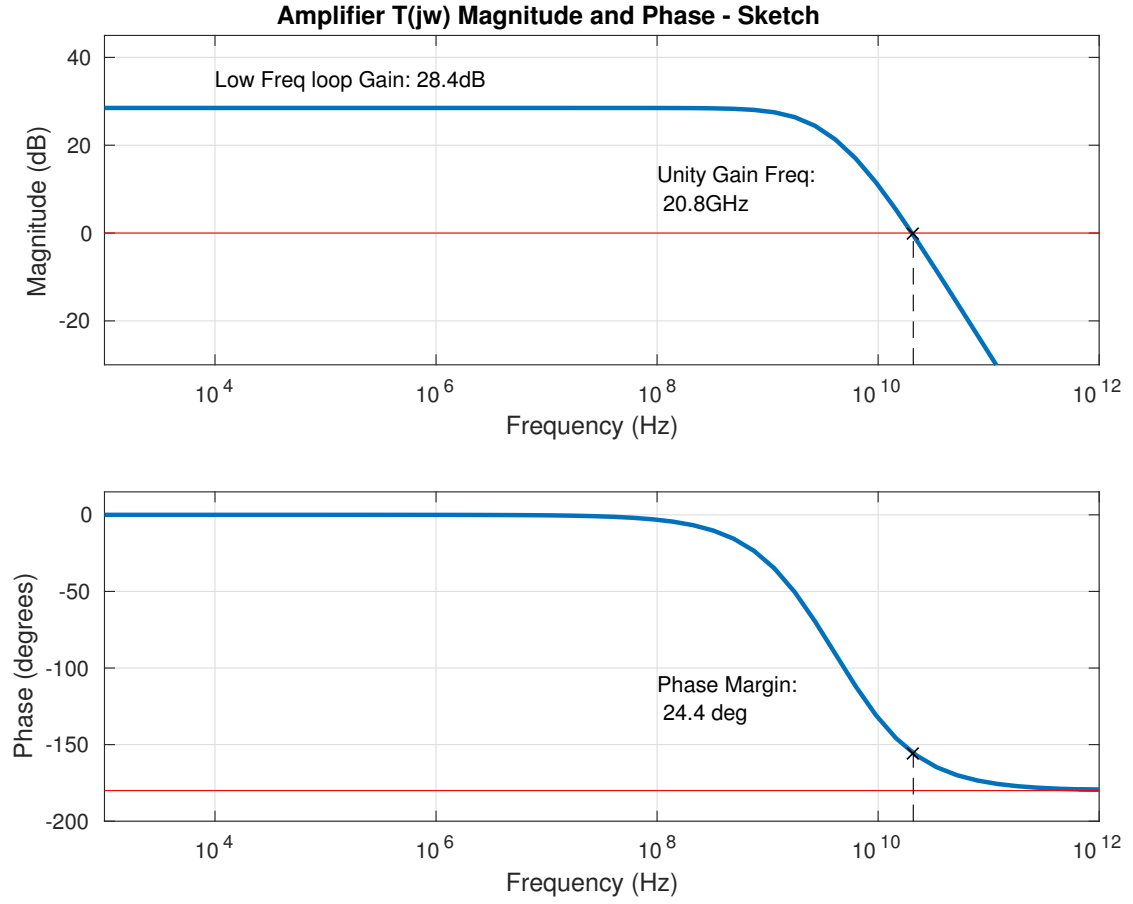(e) Calculation of  $T(j\omega)$  Unity Gain Frequency and Phase Margin

$$f_u = \sqrt{T_0 * f_{IN} * f_X} = 20.8GHz \quad (20)$$

$$PM = 180^\circ - \text{atan}\left(\frac{f_u}{f_{IN}}\right) - \text{atan}\left(\frac{f_u}{f_X}\right) = 24.4^\circ \quad (21)$$



The low value of phase margin suggests that significant peaking will be observed.

(f) Assuming a two pole loop response, the closed loop transimpedance and pole locations are given by:

$$a(s) = (R_{IN} || \frac{1}{sC_{IN}}) \cdot gm_1 \cdot (R_X || \frac{1}{sC_X}) \cdot \frac{gm_3 R_f}{1 + gm_3 R_F} \quad (22)$$

$$T(s) = \frac{T_0}{(1 + \frac{s}{\omega_X})(1 + \frac{s}{\omega_{IN}})} \quad (23)$$

$$A(s) = \frac{v_{E3}}{i_s} = \frac{a(s)}{1 + a(s)f} = \frac{1}{f} \cdot \frac{T(s)}{1 + T(s)} \quad (24)$$

Simplifying the above equation gives

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}} \quad (25)$$

where,

$$\omega_0 = \sqrt{(1 + T_0) * \omega_{IN} * \omega_X} \quad (26)$$

$$Q = \frac{\sqrt{(1 + T_0)\omega_X\omega_{IN}}}{\omega_X + \omega_{IN}} \quad (27)$$

Substituting the values of  $T_0$  and  $\omega_X$  and  $\omega_{IN}$  from parts (c) and (d) gave

$$\omega_0 = 133.32 \text{Grads}^{-1} \quad (28)$$

$$Q = 2.29 \quad (29)$$

Once  $Q$  and  $\omega_0$  are obtained, the poles are obtained by solving the equation:

$$\frac{s^2}{\omega_0^2} + \frac{s}{\omega_0 Q} + 1 = 0 \quad (30)$$


The real and imaginary pole locations obtained are


$$\text{Re}(\frac{s}{2\pi}) = -4.705 \text{GHz} \quad (31)$$

$$\text{Im}(\frac{s}{2\pi}) = 20.69 \text{GHz} \quad (32)$$

Hence the pole locations are  $(-4.705 \pm 20.69) \text{GHz}$
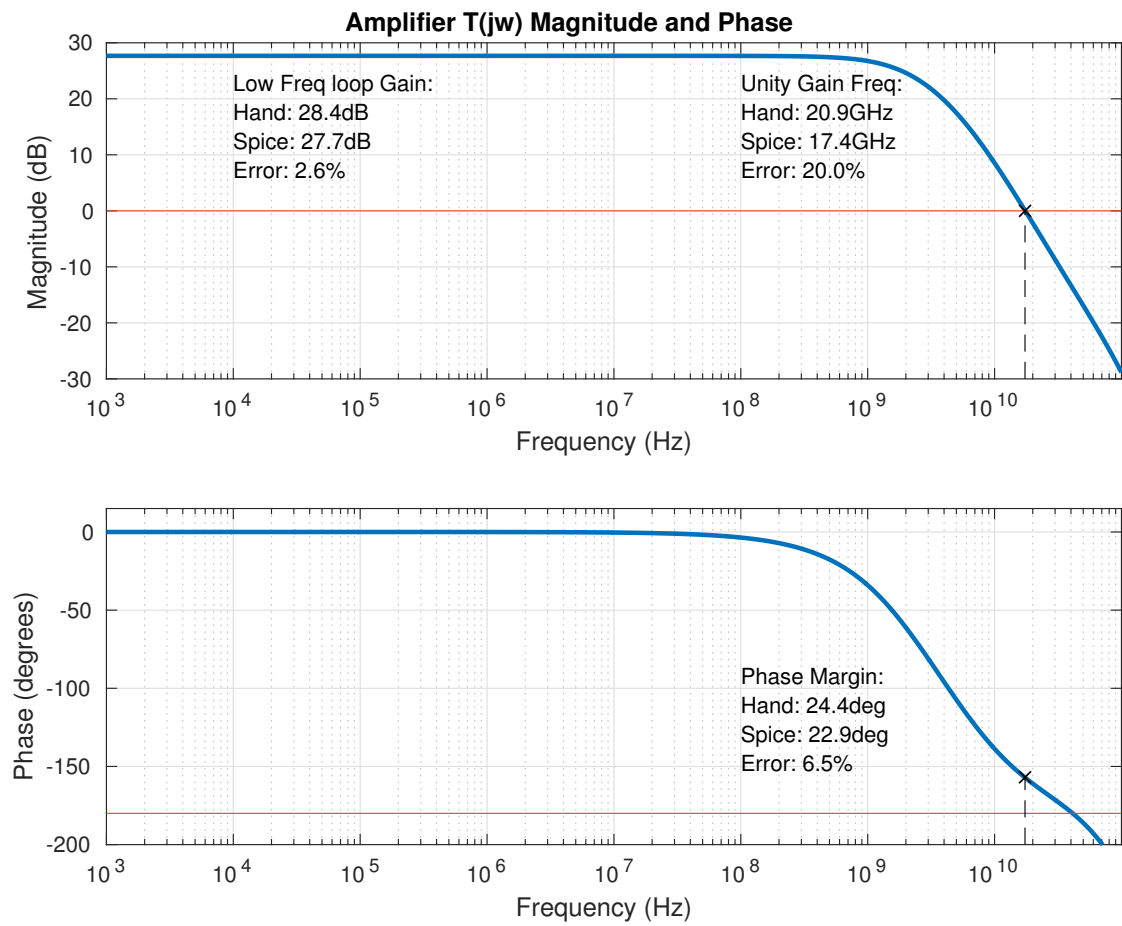
### 3 Bode Plots and PZ Outputs - Part I(g,h)



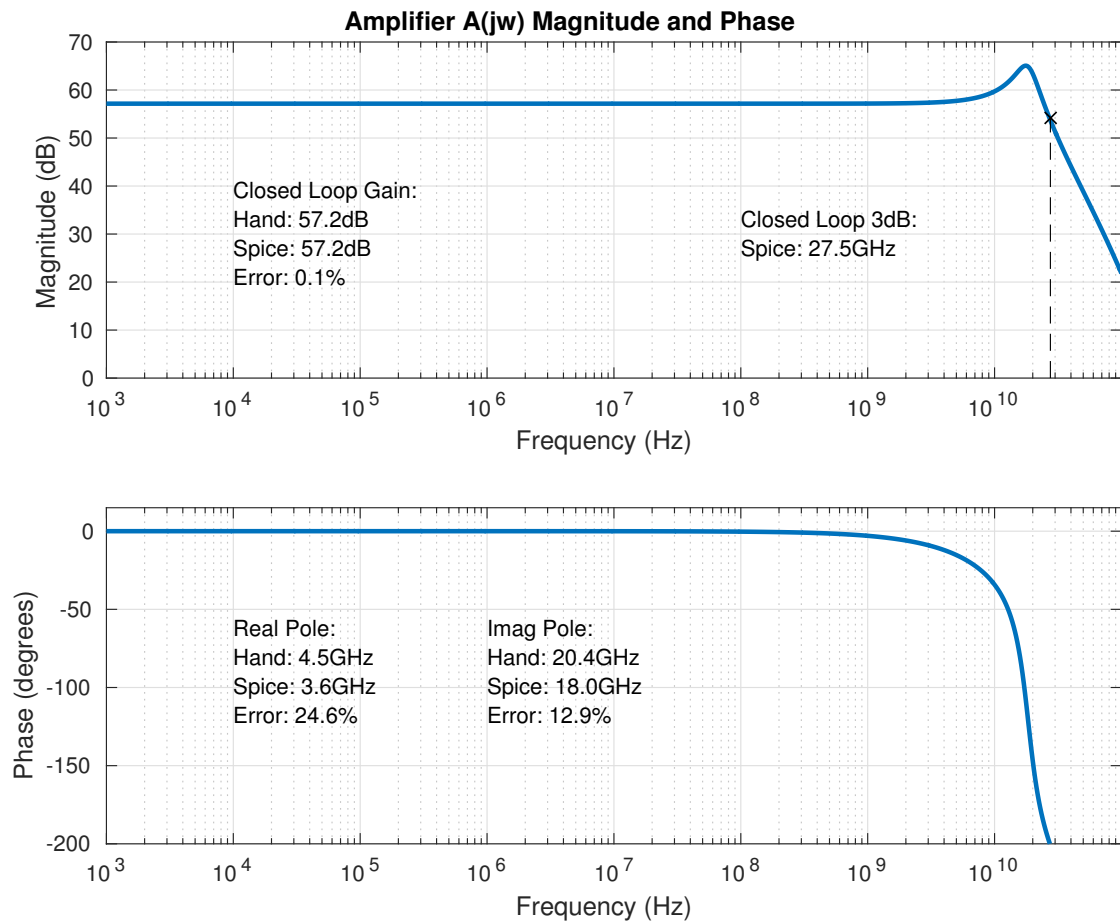

\*\*\*\*\*

\*\*\*\*\* pole/zero analysis

input = 0:is                      output = v(vo)

poles (rad/sec)                      poles ( hertz)

real	imag	real	imag
-33.1562m	0.	-5.27698m	0.
-22.9305g	113.319g	-3.64950g	18.0353g
-22.9305g	-113.319g	-3.64950g	-18.0353g
-473.782g	0.	-75.4048g	0.
-1.12800t	0.	-179.526g	0.
-1.18039t	0.	-187.865g	0.

zeros (rad/sec)

zeros ( hertz)

real	imag	real	imag
0.	0.	0.	0.
-1.10418t	0.	-175.736g	0.



## 4 Calculations for Part I(i)

A feedback capacitor can be used to introduce a zero into the feedback loop in order to push the higher frequency pole out and flatten the response of the closed loop amplifier. The optimally flat response of the amplifier occurs when  $Q = \sqrt{2}$ . Hence:

$$\omega_0 = 1.09e11 rad/s \quad (33)$$

$$\omega_Z = \frac{\omega_0}{\sqrt{2} - \frac{\omega_{P1} + \omega_{P2}}{\omega_0}} \quad (34)$$

$$C_F = \frac{1}{\omega_Z R_F} = 37 fF \quad (35)$$

From this, the new closed loop bandwidth can be calculated as such:


$$C_{in,C_F} = C_{in} + C_F \quad (36)$$


$$k = \frac{R_{in} * Q1_{gm} * R_x * A_{V3}}{R_F} \quad (37)$$

$$BW_{CL,C_F} = \frac{\sqrt{1+k}}{2\pi R_{in} C_{in} R_x C_x} = 19.2 GHz \quad (38)$$

Value of  $C_F$  was tweaked from 37fF to 45fF in order to flatten the magnitude response. Approximately 0.1dB of peaking was observed in the response curve, and with 45fF it was completely flat. We noted that on the output noise plot there was a significant bump in noise around the 3dB frequency that could be reduced by increasing  $C_F$  however this was not a specified goal of the design, so we chose to leave the value as-is.
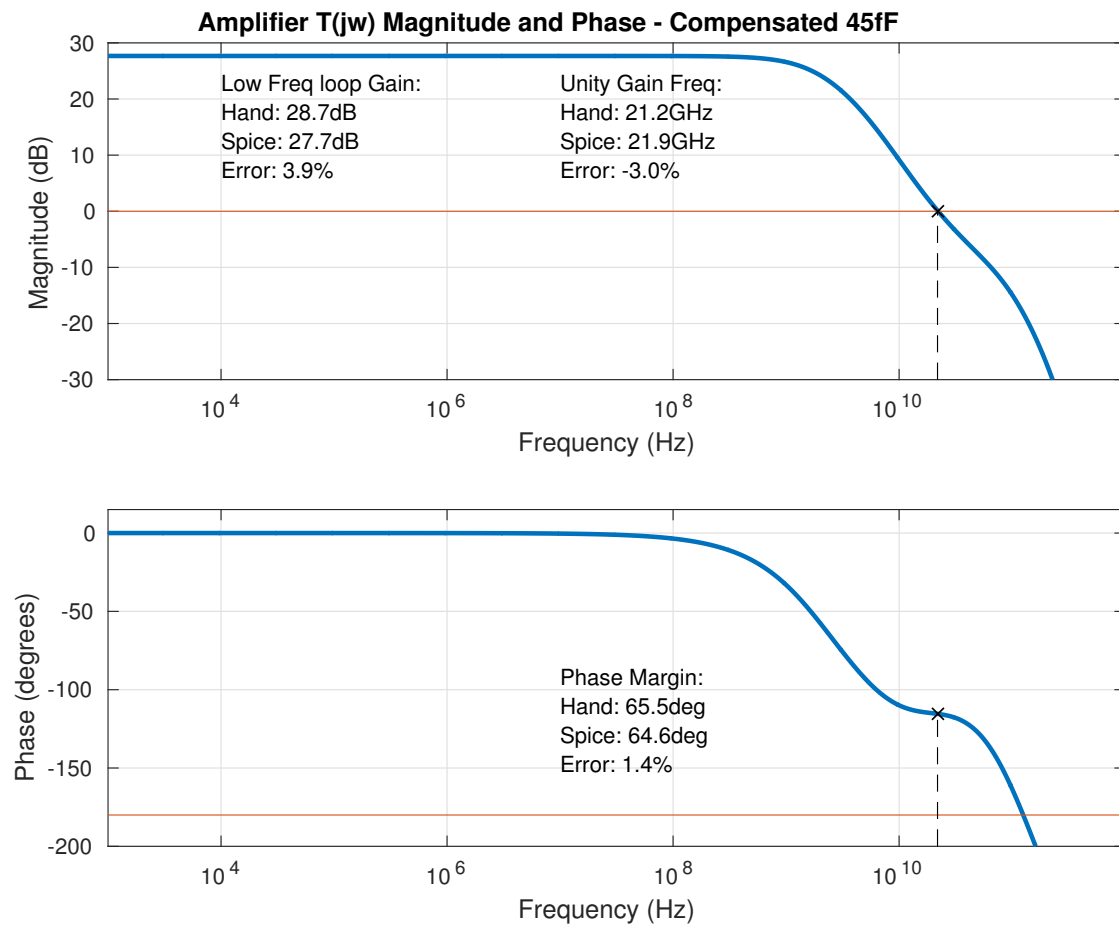
## 5 Bode Plots and PZ Outputs - Part I(j)



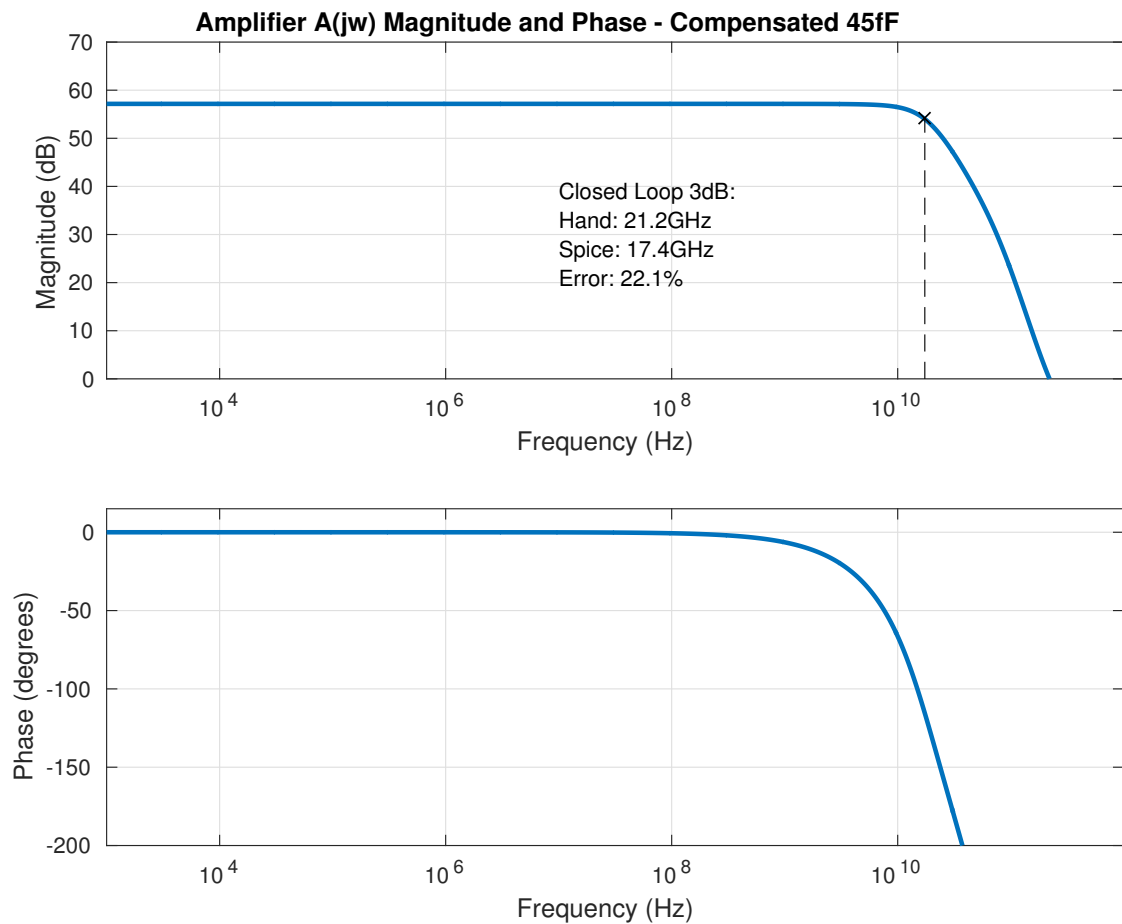

\*\*\*\*\*

\*\*\*\*\* pole/zero analysis


input = 0:is                      output = v(vo)

poles (rad/sec)		poles ( hertz)	
real	imag	real	imag
-33.1562m	0.	-5.27698m	0.
-86.5643g	75.6614g	-13.7771g	12.0419g
-86.5643g	-75.6614g	-13.7771g	-12.0419g
-385.396g	343.565g	-61.3377g	54.6800g
-385.396g	-343.565g	-61.3377g	-54.6800g
-1.11884t	0.	-178.069g	0.
-1.35144t	0.	-215.088g	0.
-1.90665t	0.	-303.452g	0.

zeros (rad/sec)		zeros ( hertz)	
real	imag	real	imag
0.	0.	0.	0.
-1.09715t	0.	-174.617g	0.

## 6 Noise - Part I(k,l)

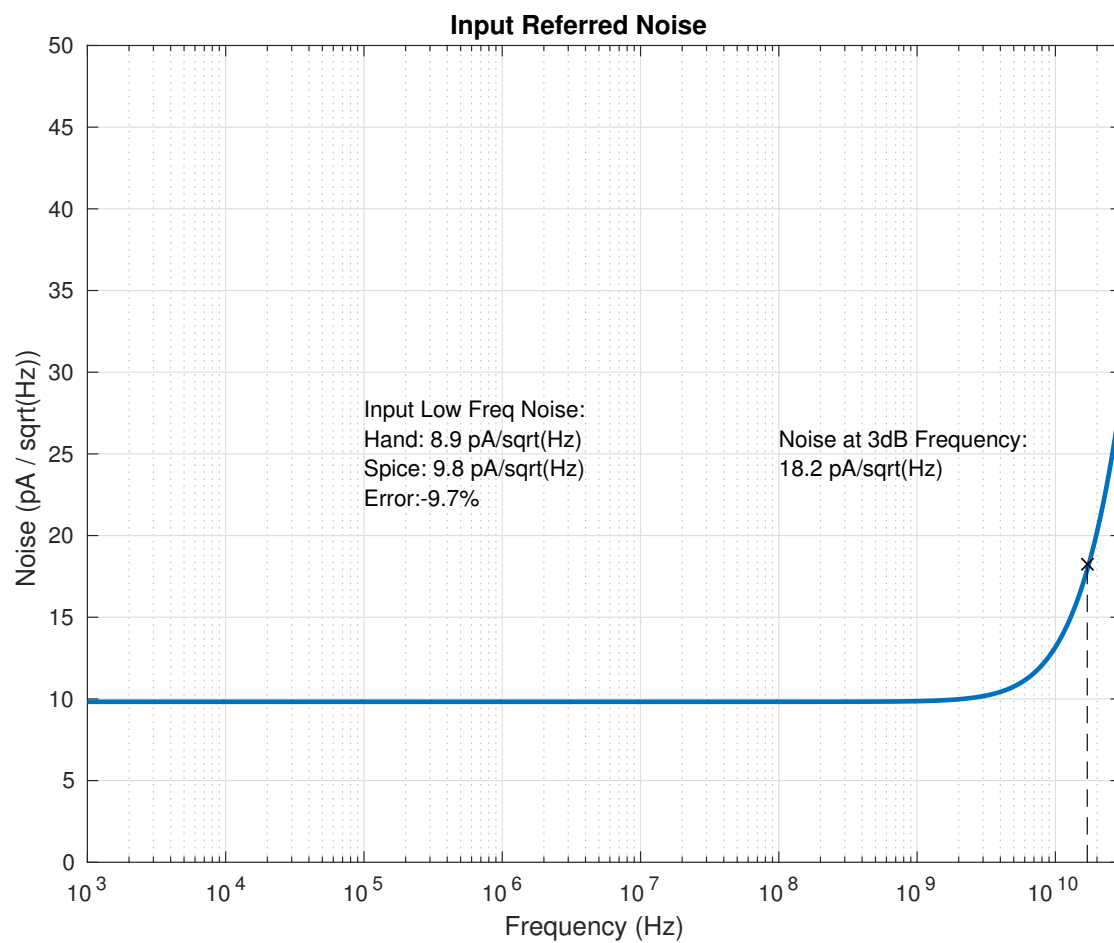

## 7 Transient Response - Part I(m)

