

2016 EE214B Design Project - Part I

Singireddy, Sanjana
sanjana9@stanford.edu
SUID:06030068

Lenius, Samuel
lenius@stanford.com
SUID:06091240

February 28, 2016

1 Bias Calculations

1.1 Node Definitions

$$V_{C1} = V_{E2} = V_W$$

$$V_{B3} = V_{C2} = V_{B4} = V_X$$

$$V_{E3} = V_Y$$

$$V_{E4} = V_Z$$

$$V_{B1} = V_{IN}$$

1.2 Node Voltages and Device Currents

$$V_{IN} = V_{BE} = 0.8V \quad (1)$$

$$V_{B2} = 1.6V \Rightarrow V_W = 1.6 - V_{BE} = 0.8V \quad (2)$$

Assuming $I_b = 0$

$$V_{IN} = V_Y \Rightarrow V_Y = 0.8V \quad (3)$$

$$V_X = V_Y + V_{BE} \Rightarrow V_X = 1.6V \quad (4)$$

$$V_Z = V_X - V_{BE} \Rightarrow V_Z = 0.8V \quad (5)$$

$$V_O = V_{CC} - IB4R_{C4} \Rightarrow V_O = 2.3V \quad (6)$$

$$I_{C1} = I_{C2} = \frac{V_{CC} - V_{B3}}{R_{C2}} = 3.6mA \quad (7)$$

$$I_{C3} = I_{Bias3} = 4.5mA \quad (8)$$

$$I_{C4} = I_{Bias4} = 2.0mA \quad (9)$$

| Parameter | Hand Calc | Spice Value | Percent Error% |
|-----------|----------------|-----------------|----------------|
| V_{IN} | 0.800V | 0.801V | -0.12% |
| V_W | 0.800V | 0.798V | 0.25% |
| V_X | 1.600V | 1.605V | -0.31% |
| V_Y | 0.800V | 0.804V | -0.49% |
| V_Z | 0.800V | 0.813V | -1.50% |
| V_O | 2.300V | 2.301V | -0.04% |
| gm_1 | 120.7mS | 120.7mS | -0.03% |
| gm_2 | 120.3mS | 120.3mS | -0.03% |
| gm_3 | 152.3mS | 152.3mS | 0.02% |
| gm_4 | 70mS | 70mS | -0.04% |
| $r\pi_1$ | 2.14k Ω | 1.875k Ω | 14.3% |
| $r\pi_2$ | 2.14k Ω | 1.883k Ω | 13.64% |
| $r\pi_3$ | 1.71k Ω | 1.502k Ω | 13.84% |
| $r\pi_4$ | 3.85k Ω | 3.515k Ω | 9.5% |

2 Calculations and plots for part I (c) through (f)

After applying two-port analysis for loop gain calculation:

$$a = (r_{\pi 1} || R_F) \cdot (-gm_1 R_{C2}) \cdot \frac{gm_3 R_F}{1 + gm_3 R_F} = -5.486k\Omega \quad (10)$$

$$f = \frac{-1}{R_F} = -4.5mS \quad (11)$$

$$t = af = 26.57 = 28.48dB \quad (12)$$

Mid-band transresistance of the overall amplifier:

$$A_{CL, MidB and} = \frac{a}{1 + t} \cdot \frac{-gm_4 R_{C4}}{1 + gm_4 R_{E4}} = 724 = 57.2dB \quad (13)$$

Calculating node resistances and capacitances:

$$C_X = C_{\mu 2} + \frac{C_{\pi 3}}{1 + gm_3 R_F} + \frac{C_{\pi 4}}{1 + gm_4 R_{E4}} + C_{\mu 3} + C_{\mu 4}(1 + gm_4 R_{C4}) = 99fF \quad (14)$$

$$R_X = R_{C2} || r_{\pi 3}(1 + gm_3 R_F) || r_{\pi 4}(1 + gm_4 R_{E4}) = 241\Omega \approx R_{C2} \quad (15)$$

$$C_{IN} = C_D + C_{\pi 1} + C_{\mu 1} = 324fF \quad (16)$$

$$R_{IN} = r_{\pi 1} || R_F = 199\Omega \approx R_F \quad (17)$$

Calculation of most significant poles:


$$f_{IN} = \frac{1}{2\pi R_{IN} C_{IN}} = 2.46GHz \quad (18)$$

$$f_X = \frac{1}{2\pi R_X C_X} = 6.63GHz \quad (19)$$

Calculation of $T(j\omega)$ Unity Gain Frequency and Phase Margin

$$f_u = \sqrt{T_0 * f_{IN} * f_X} = 20.8GHz \quad (20)$$
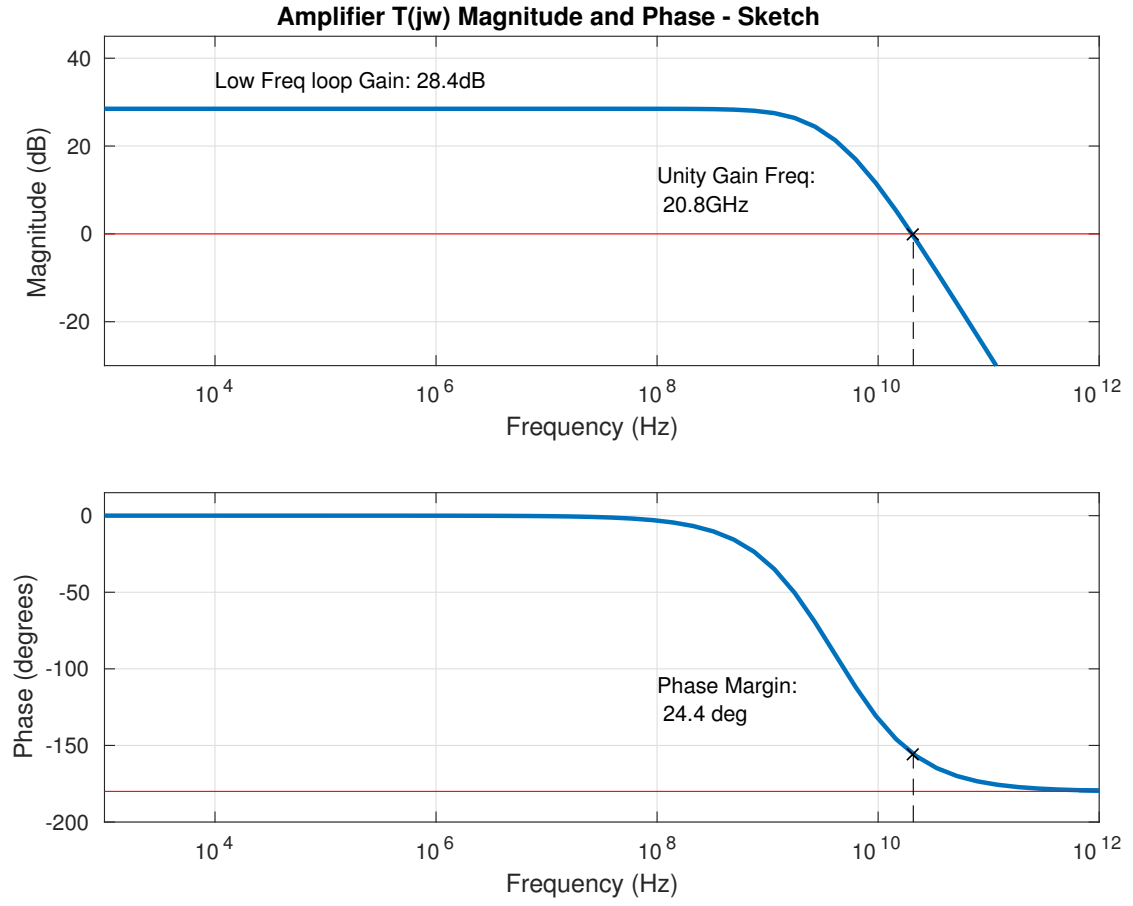
$$PM = 180^\circ - atan(\frac{f_u}{f_{IN}}) - atan(\frac{f_u}{f_X}) = 24.4^\circ \quad (21)$$



The low value of phase margin suggests that significant peaking will be observed.

$$a(s) = (R_{IN} || \frac{1}{sC_{IN}}) \cdot gm_1 \cdot (R_X || \frac{1}{sC_X}) \cdot \frac{gm_3 R_f}{1 + gm_3 R_F} \quad (22)$$

$$\frac{v_{E3}}{i_s} = \frac{a(s)}{1 + a(s)f} \quad (23)$$


$$f_0 = \sqrt{(1 + T_0) * f_{IN} * f_X} \approx f_u \quad (24)$$


$$Q = \frac{\sqrt{(1 + T_0)\omega_X\omega_{IN}}}{\omega_X + \omega_{IN}} = 2.29 \quad (25)$$

(page intentionally left blank)

(page intentionally left blank)

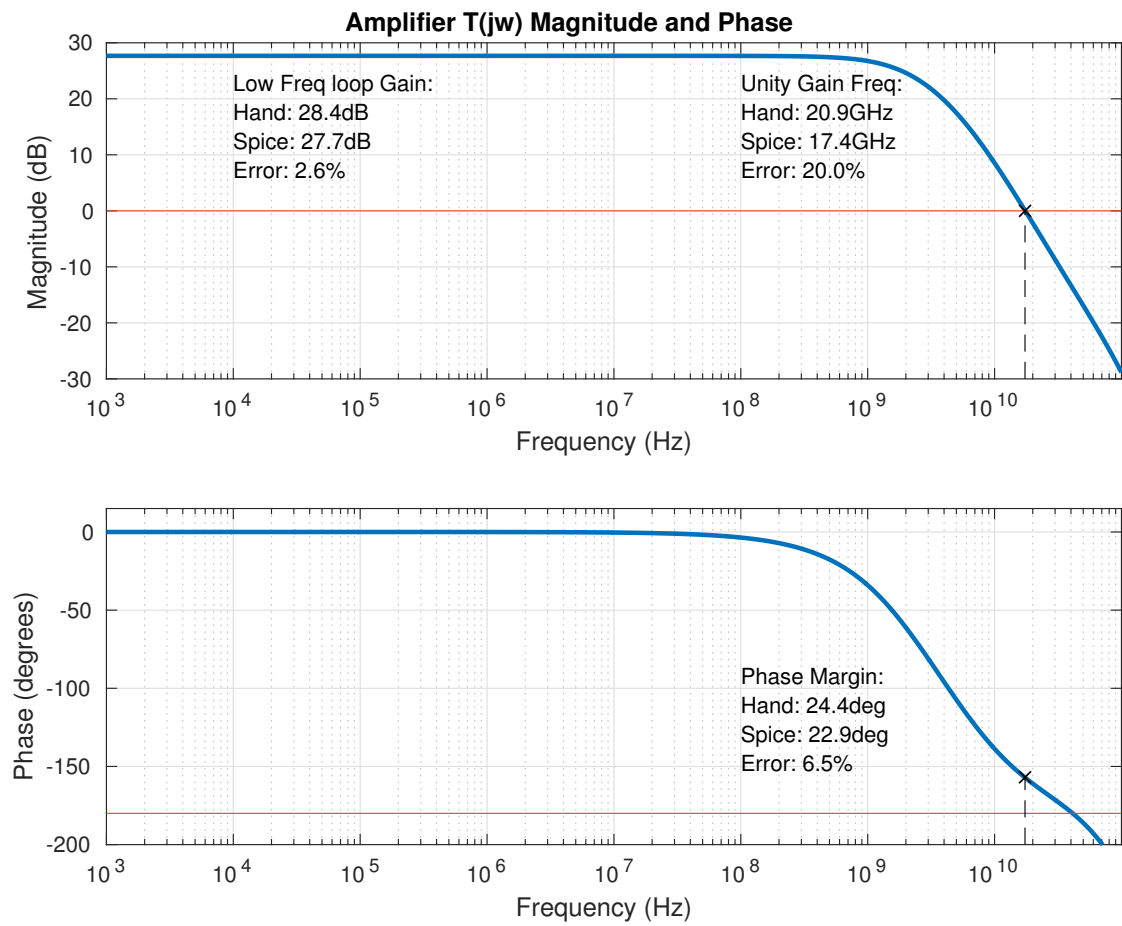3 Bode Plots and PZ Outputs - Part I(g,h)



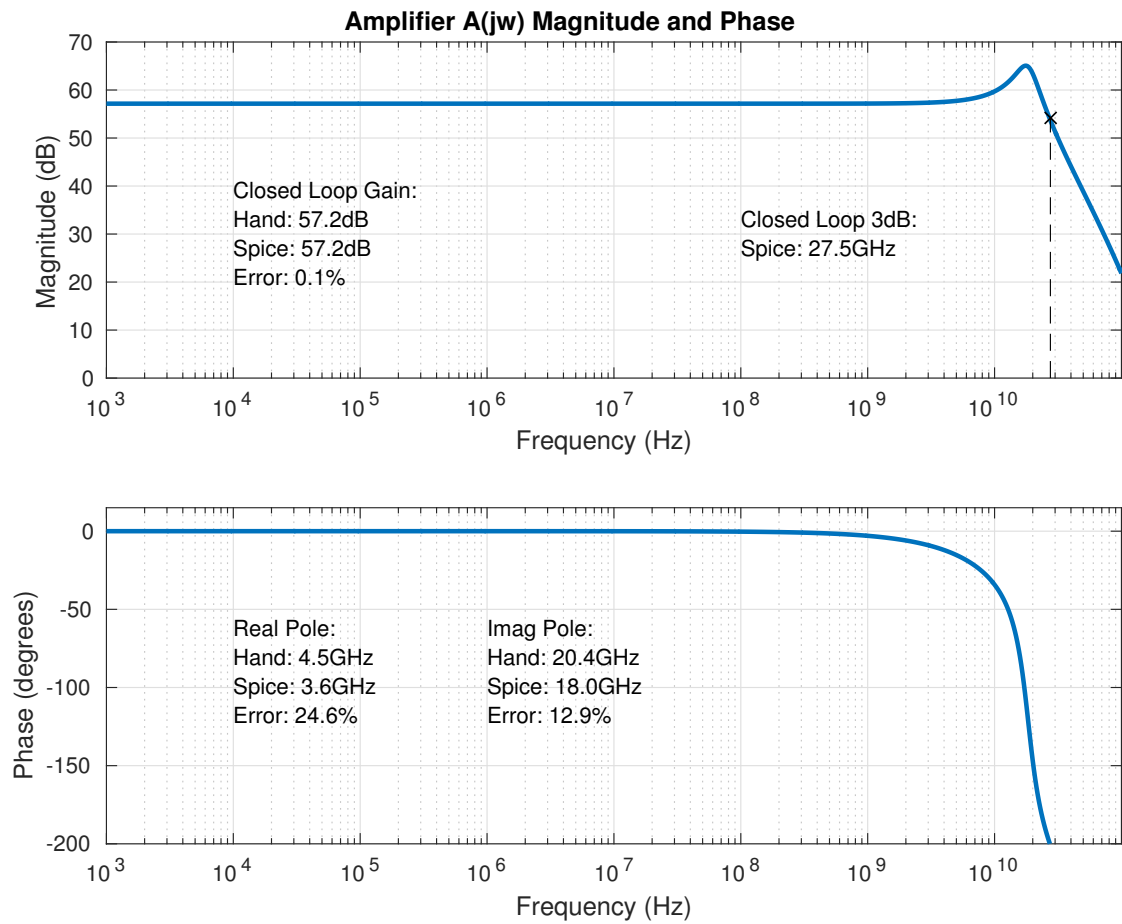

***** pole/zero analysis

input = 0:is output = v(vo)

poles (rad/sec) poles (hertz)

| real | imag | real | imag |
|-----------|-----------|-----------|-----------|
| -33.1562m | 0. | -5.27698m | 0. |
| -22.9305g | 113.319g | -3.64950g | 18.0353g |
| -22.9305g | -113.319g | -3.64950g | -18.0353g |
| -473.782g | 0. | -75.4048g | 0. |
| -1.12800t | 0. | -179.526g | 0. |
| -1.18039t | 0. | -187.865g | 0. |

zeros (rad/sec)

zeros (hertz)

| real | imag | real | imag |
|-----------|------|-----------|------|
| 0. | 0. | 0. | 0. |
| -1.10418t | 0. | -175.736g | 0. |

4 Calculations for Part I(i)

A feedback capacitor can be used to introduce a zero into the feedback loop in order to push the higher frequency pole out and flatten the response of the closed loop amplifier. The optimally flat response of the amplifier occurs when $Q = \sqrt{2}$. Hence:

$$\omega_0 = 1.09e11 rad/s \quad (26)$$

$$\omega_Z = \frac{\omega_0}{\sqrt{2} - \frac{\omega_{P1} + \omega_{P2}}{\omega_0}} \quad (27)$$

$$C_F = \frac{1}{\omega_Z R_F} = 37 fF \quad (28)$$

From this, the new closed loop bandwidth can be calculated as such:


$$C_{in,C_F} = C_{in} + C_F \quad (29)$$


$$k = \frac{R_{in} * Q1_{gm} * R_x * A_{V3}}{R_F} \quad (30)$$

$$BW_{CL,C_F} = \frac{\sqrt{1+k}}{2\pi R_{in} C_{in} R_x C_x} = 19.2 GHz \quad (31)$$

Value of C_F was tweaked from 37fF to 45fF in order to flatten the magnitude response. Approximately 0.1dB of peaking was observed in the response curve, and with 45fF it was completely flat. We noted that on the output noise plot there was a significant bump in noise around the 3dB frequency that could be reduced by increasing C_F however this was not a specified goal of the design, so we chose to leave the value as-is.

5 Bode Plots and PZ Outputs - Part I(j)

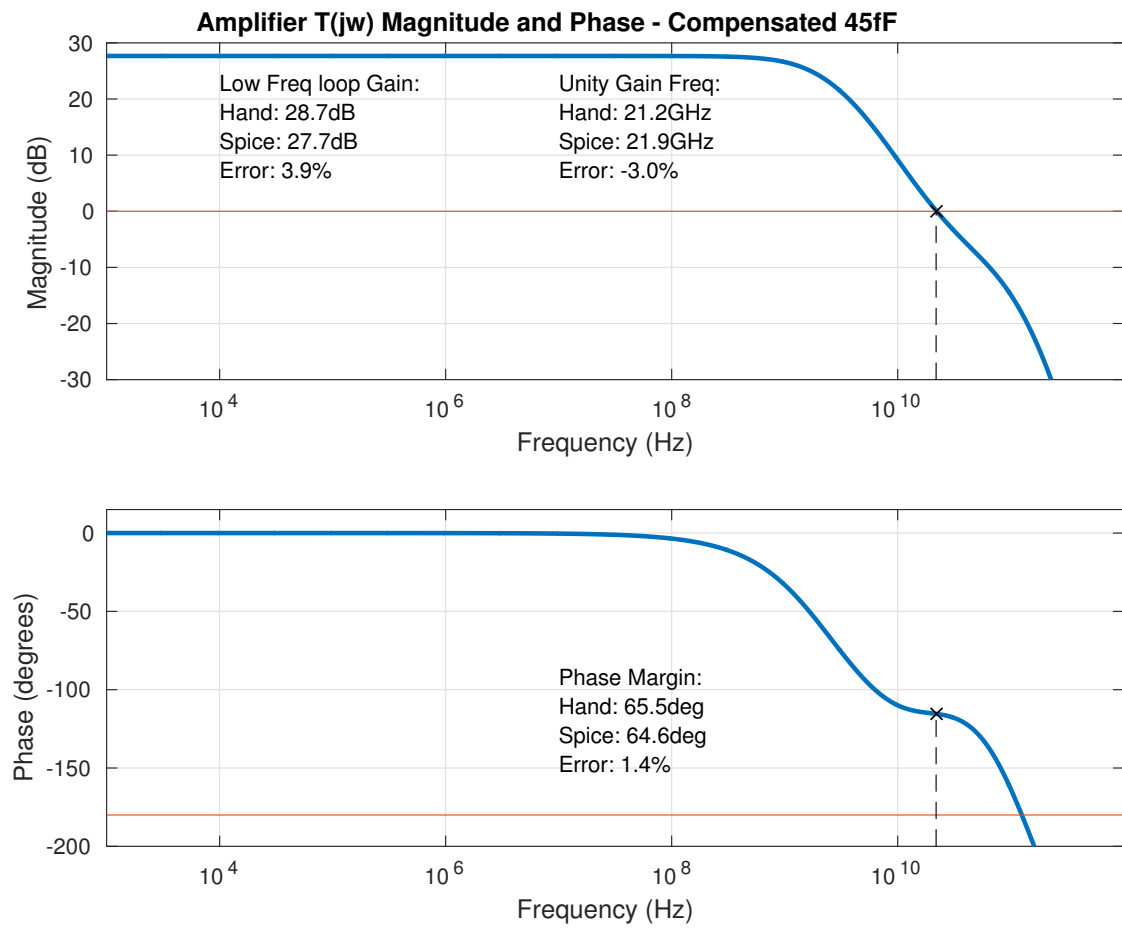

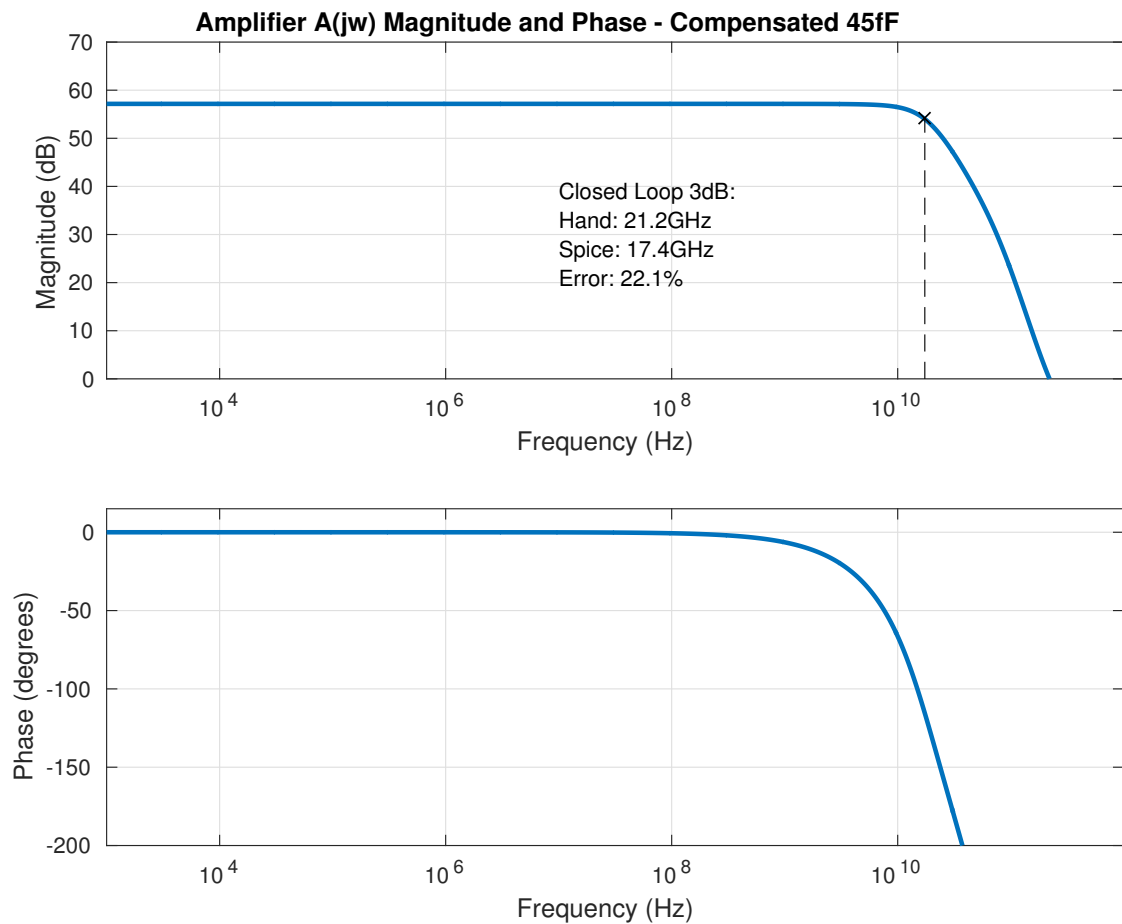


***** pole/zero analysis

input = 0:is output = v(vo)

| poles (rad/sec) | | poles (hertz) | |
|-----------------|-----------|----------------|-----------|
| real | imag | real | imag |
| -33.1562m | 0. | -5.27698m | 0. |
| -86.5643g | 75.6614g | -13.7771g | 12.0419g |
| -86.5643g | -75.6614g | -13.7771g | -12.0419g |
| -385.396g | 343.565g | -61.3377g | 54.6800g |
| -385.396g | -343.565g | -61.3377g | -54.6800g |
| -1.11884t | 0. | -178.069g | 0. |
| -1.35144t | 0. | -215.088g | 0. |
| -1.90665t | 0. | -303.452g | 0. |

| zeros (rad/sec) | | zeros (hertz) | |
|-----------------|------|----------------|------|
| real | imag | real | imag |
| 0. | 0. | 0. | 0. |
| -1.09715t | 0. | -174.617g | 0. |

6 Noise - Part I(k,l)

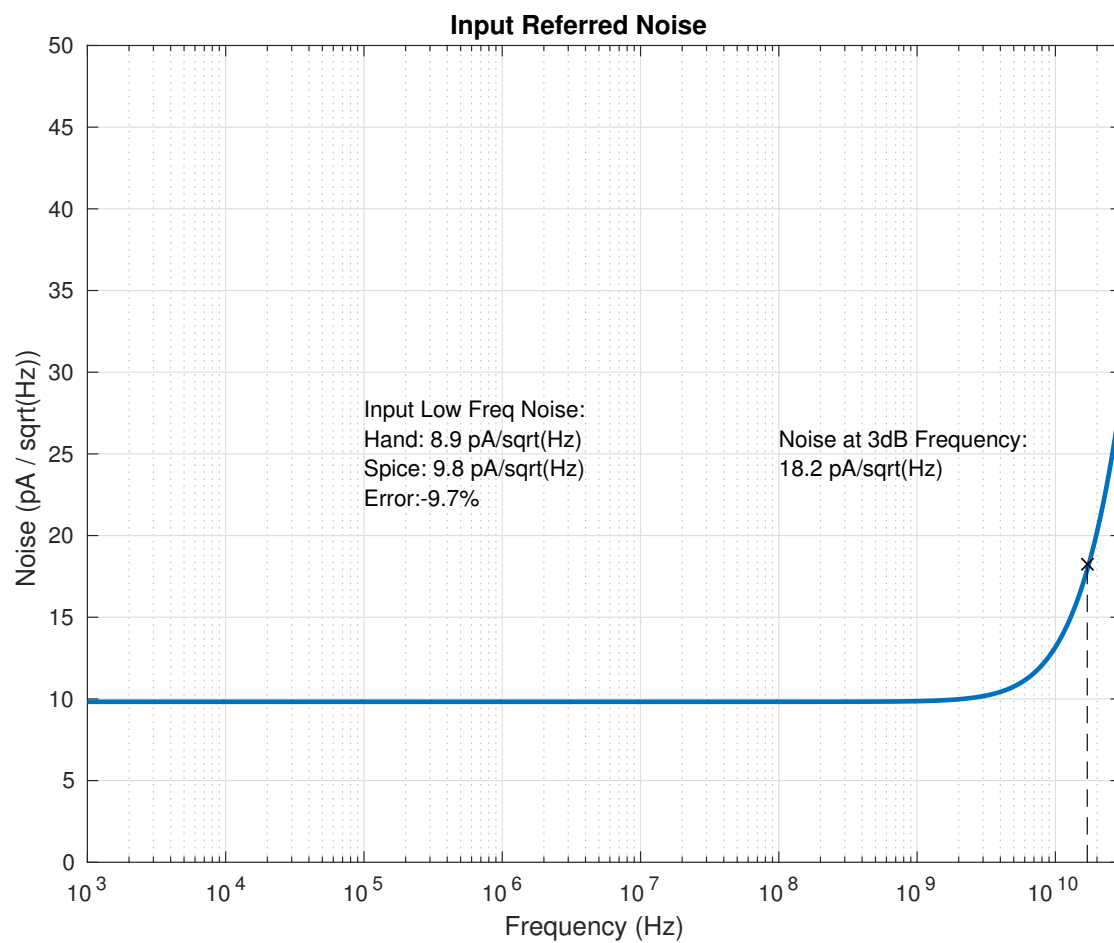

7 Transient Response - Part I(m)

